



Power Accelerated

State-of-the-Art Mobile Charging: Topologies, Technologies and Performance

PSMA Industry Session IS05: Mobile Applications

Tom Ribarich, Dir. Systems Engineering, tom.ribarich@navitassemi.com


Stephen Oliver, VP Sales & Marketing, stephen.oliver@navitassemi.com

March 29th 2017


Getting to Fast...

- Topology / technique
 - Hard-switch → Soft switch (ZVS)
 - New technology enables new topologies to be commercially viable
- Switch technology
 - Si Bipolar → Si FET → Discrete / Cascoded GaN → GaN Power ICs
- Magnetic Materials
 - New compounds / alloys, optimized for high frequency

Fast → Small

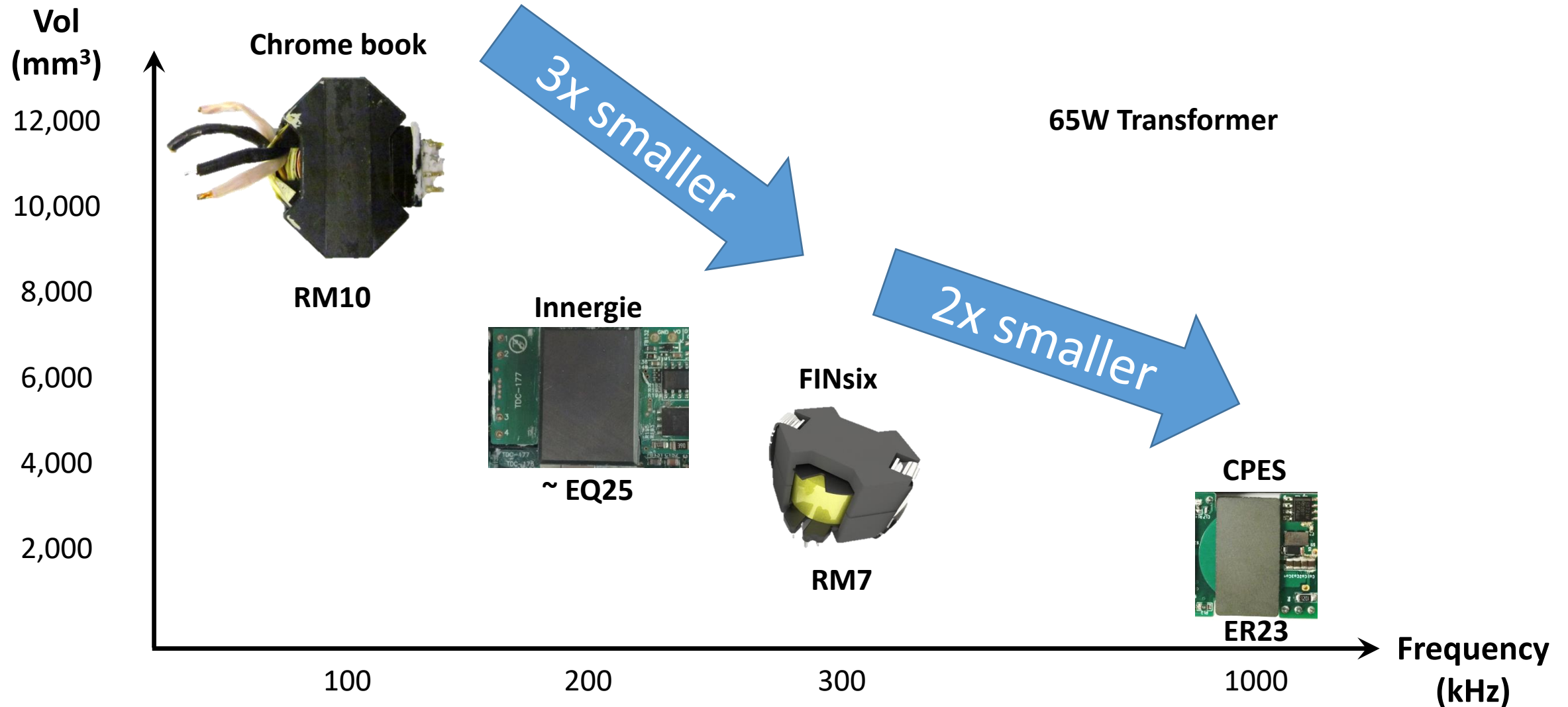


Adapter Density 2016:

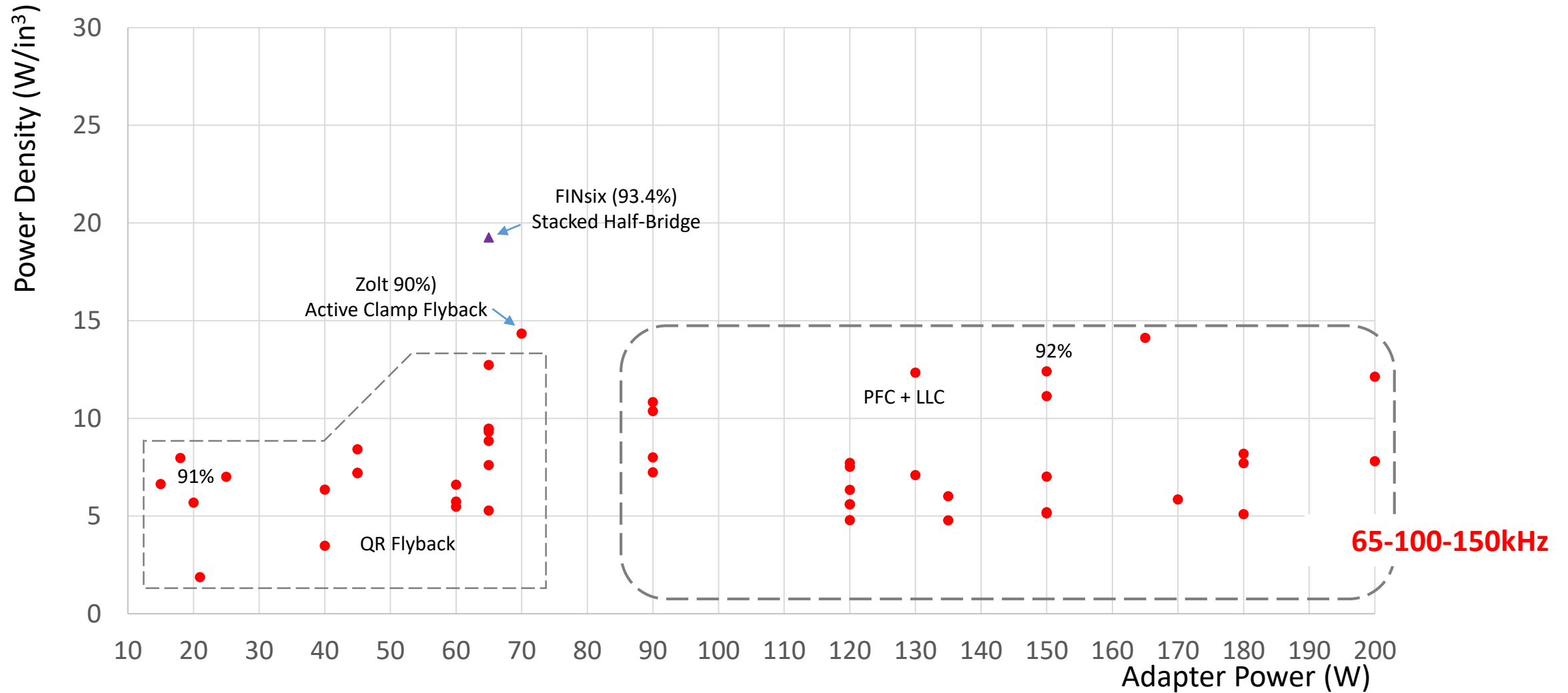


65-100-150kHz

Frequency Drives Size

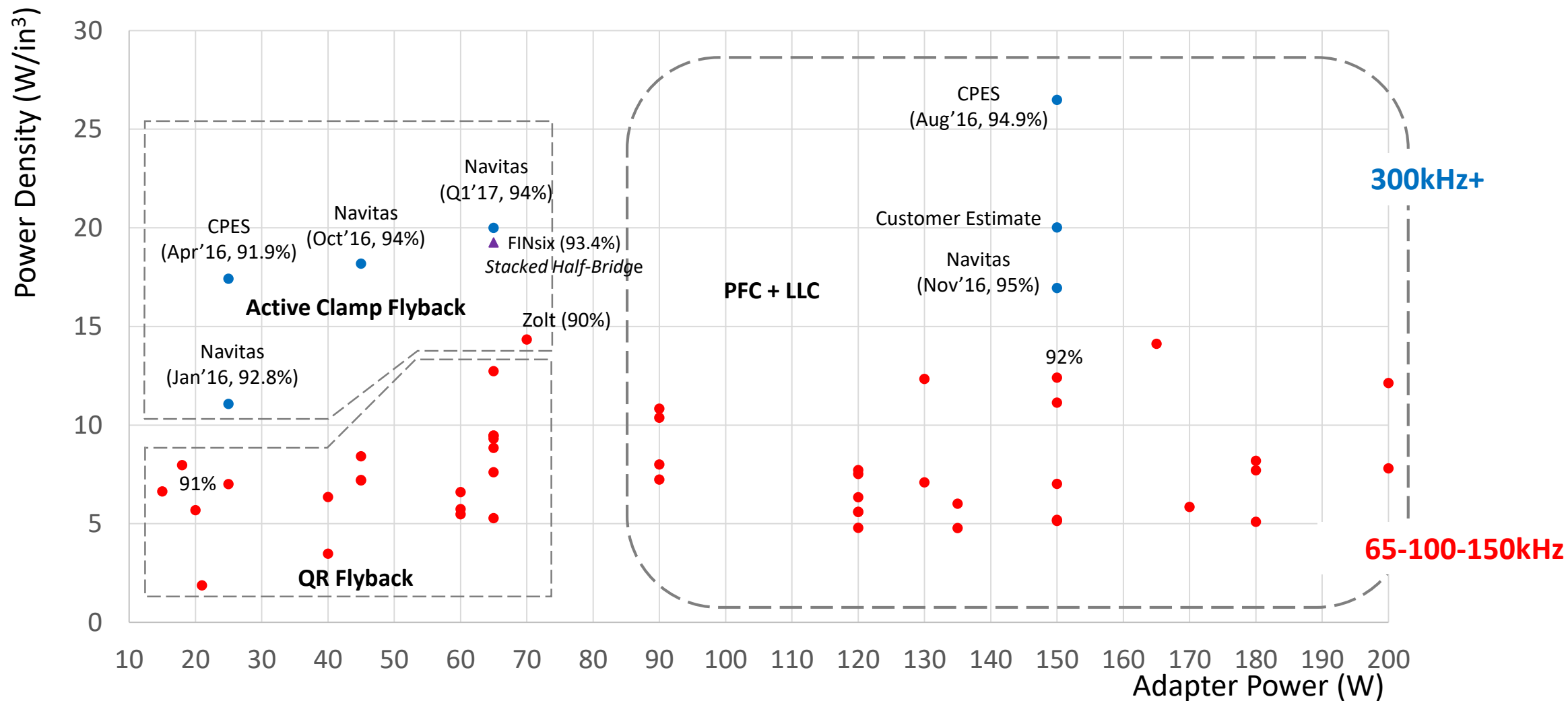


-

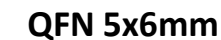

GaN Power IC – *Fast & Efficient*

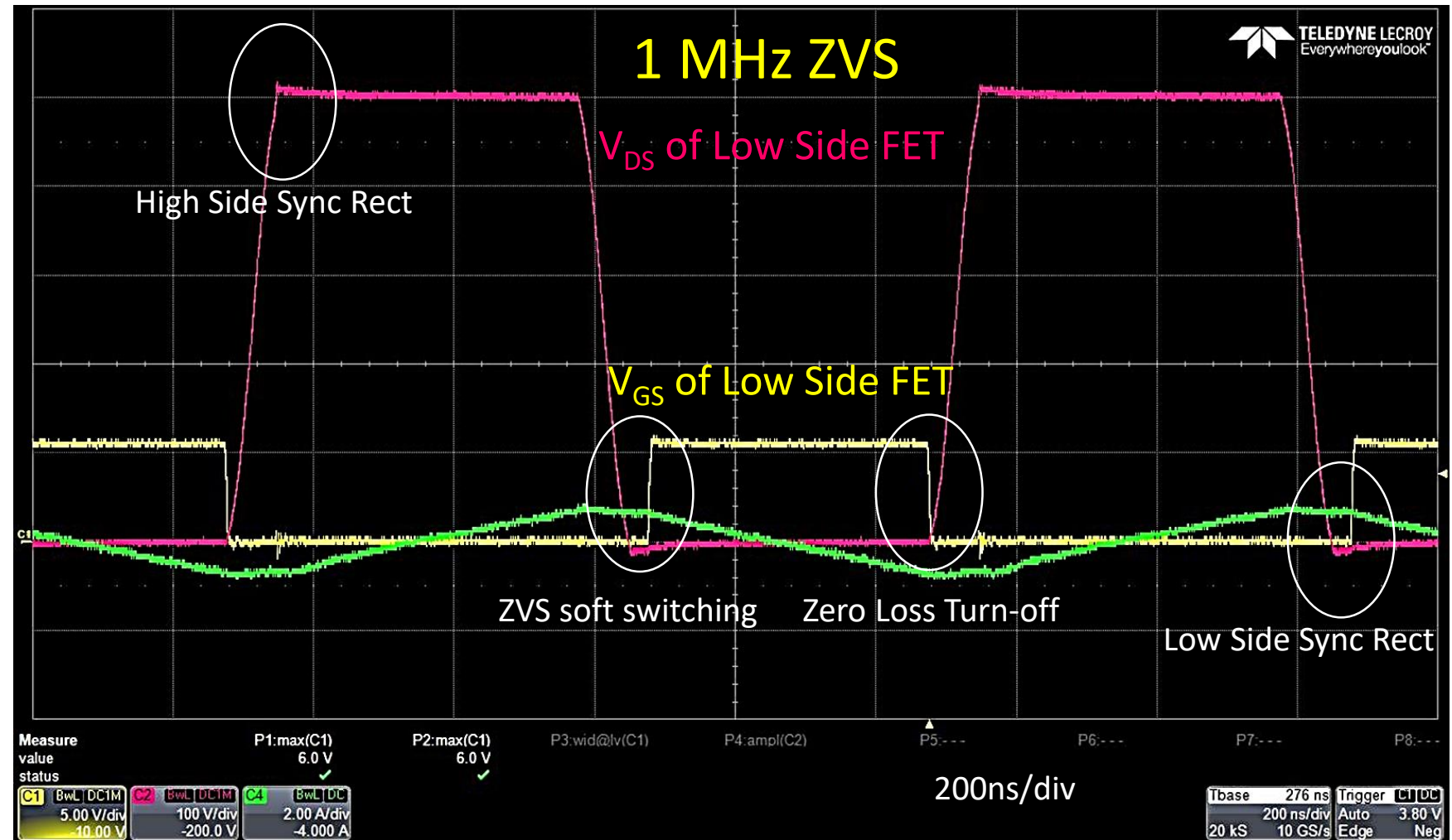
- 500 V Switching
- No overshoot / spike
- No oscillations
- ‘S-curve’ transitions
- Zero Loss Turn-on
- Zero Loss Turn-off
- Sync Rectification
- High frequency
- Small, low cost magnetics



Half-Bridge iDrive GaN Power IC




PQFN 6x8 mm

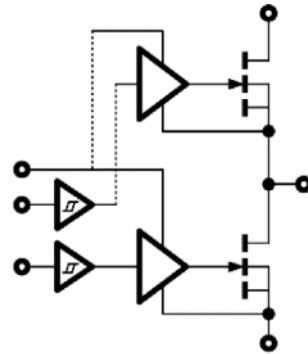



Simplified Schematic

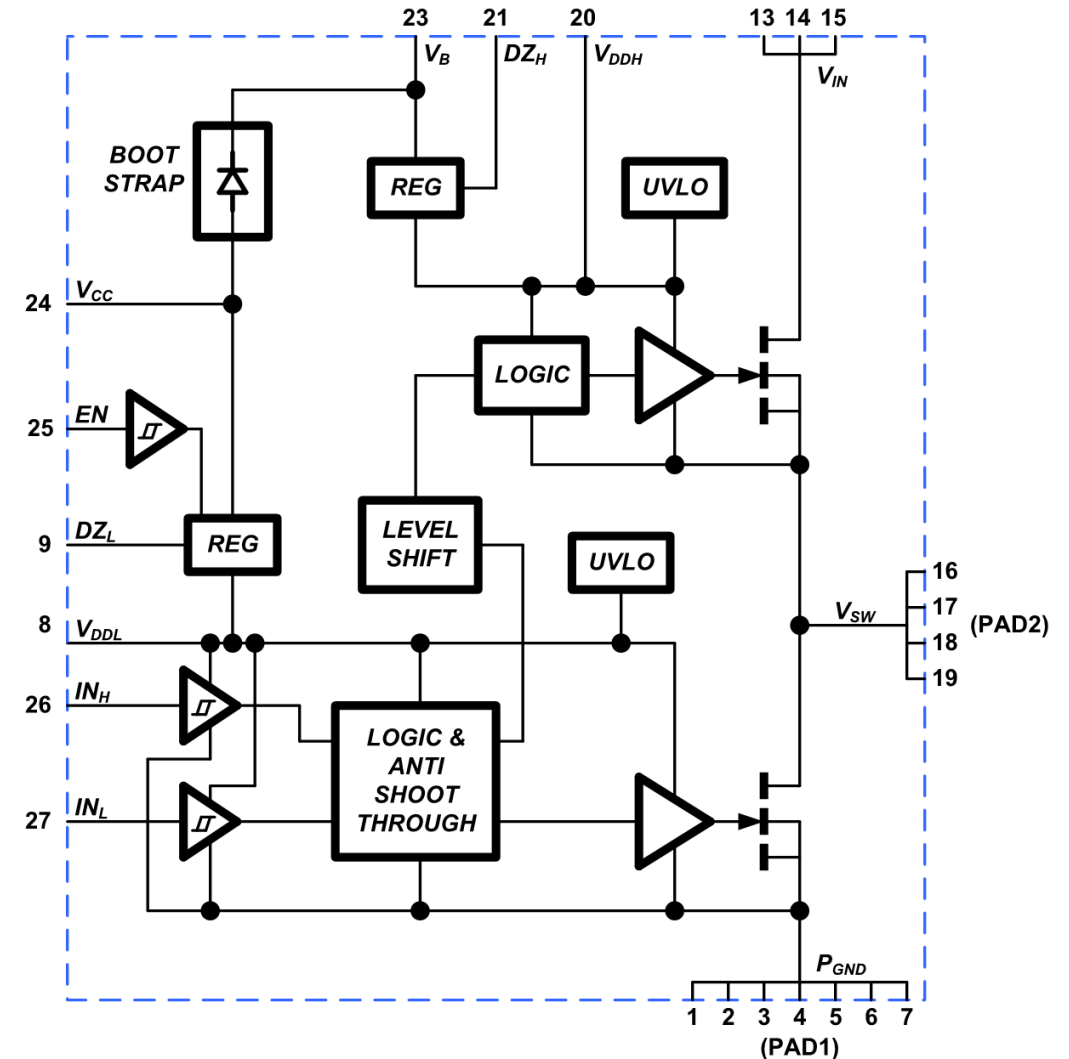- Internal level-shift, bootstrap
- Range from (2x) 160-560 mOhm (650V)
- Single component
- Ground-referenced control
- Active Clamp Flyback, Half-Bridge, LLC, etc.





High Frequency Magnetics

N59 optimized for 2MHz

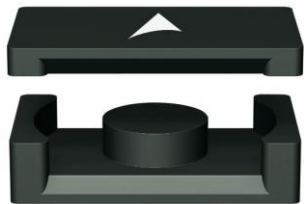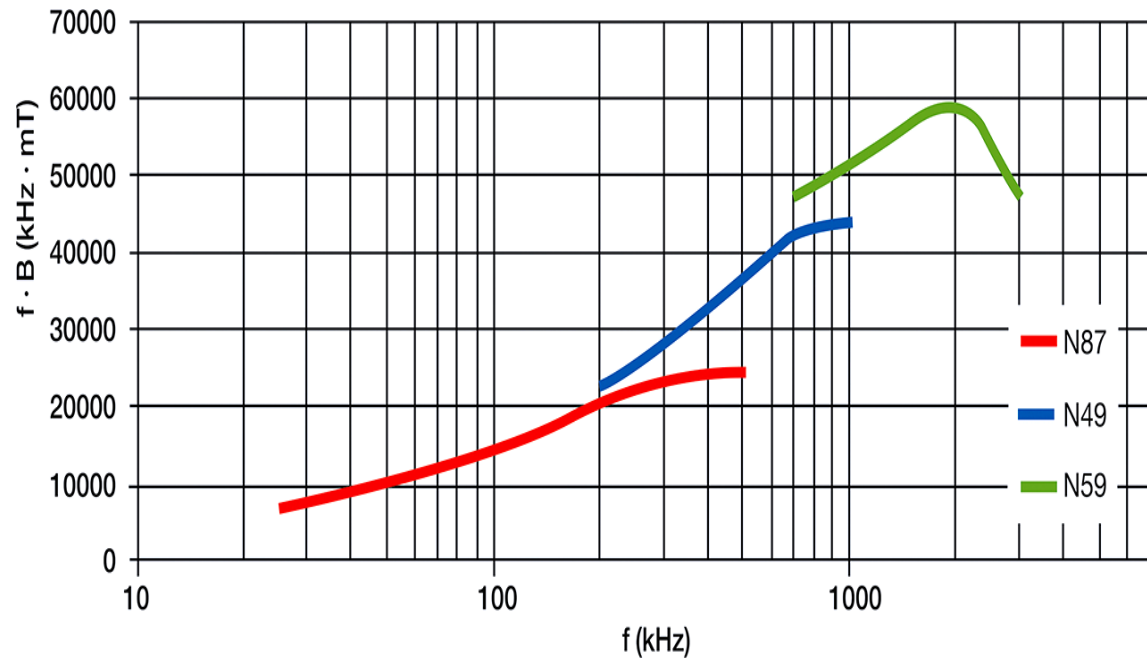

3F & 4F up to 10MHz

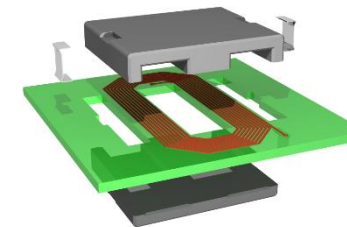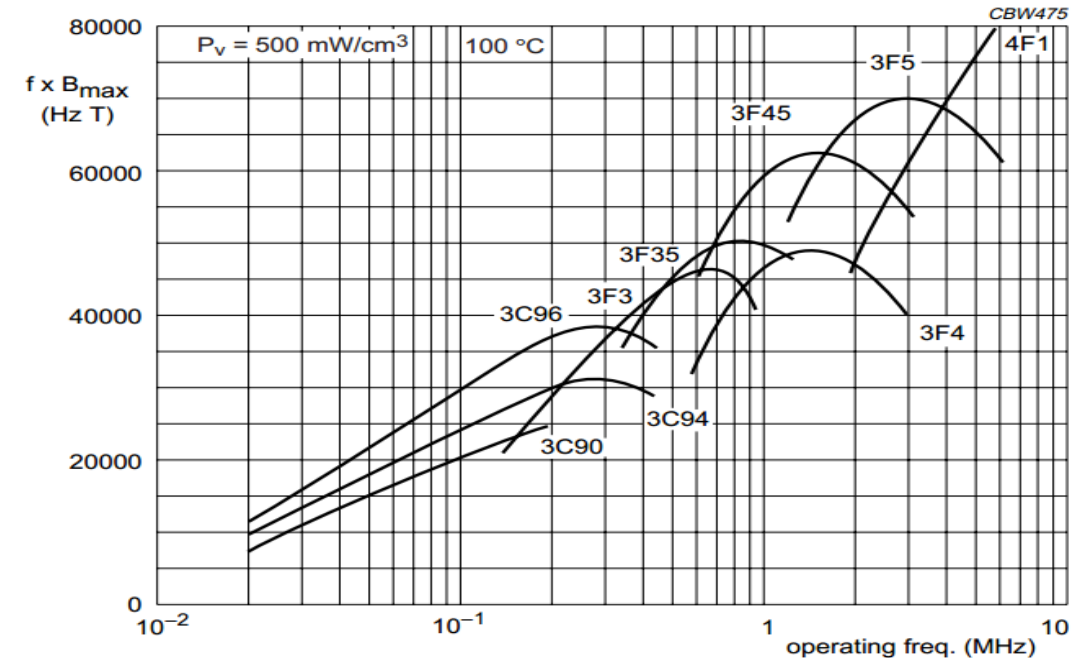


TDK/EPCOS N59/PC200
Hitachi Metals ML91S
ACME P61



: <https://en.tdk.eu/tdk-en/374108/tech-library/articles/products---technologies/products---technologies/low-losses-at-high-frequencies/1206400>
: <http://www.hitachi-metals.co.jp/e/press/news/2016/n0404.html>
: <http://www.acme-ferrite.com.tw/en/material.asp>, <http://www.acme-ferrite.com.tw/investor/m3.pdf>

Fast Chargers ... going "GaN Fast"



3x Fast Charging with 50% Energy Savings

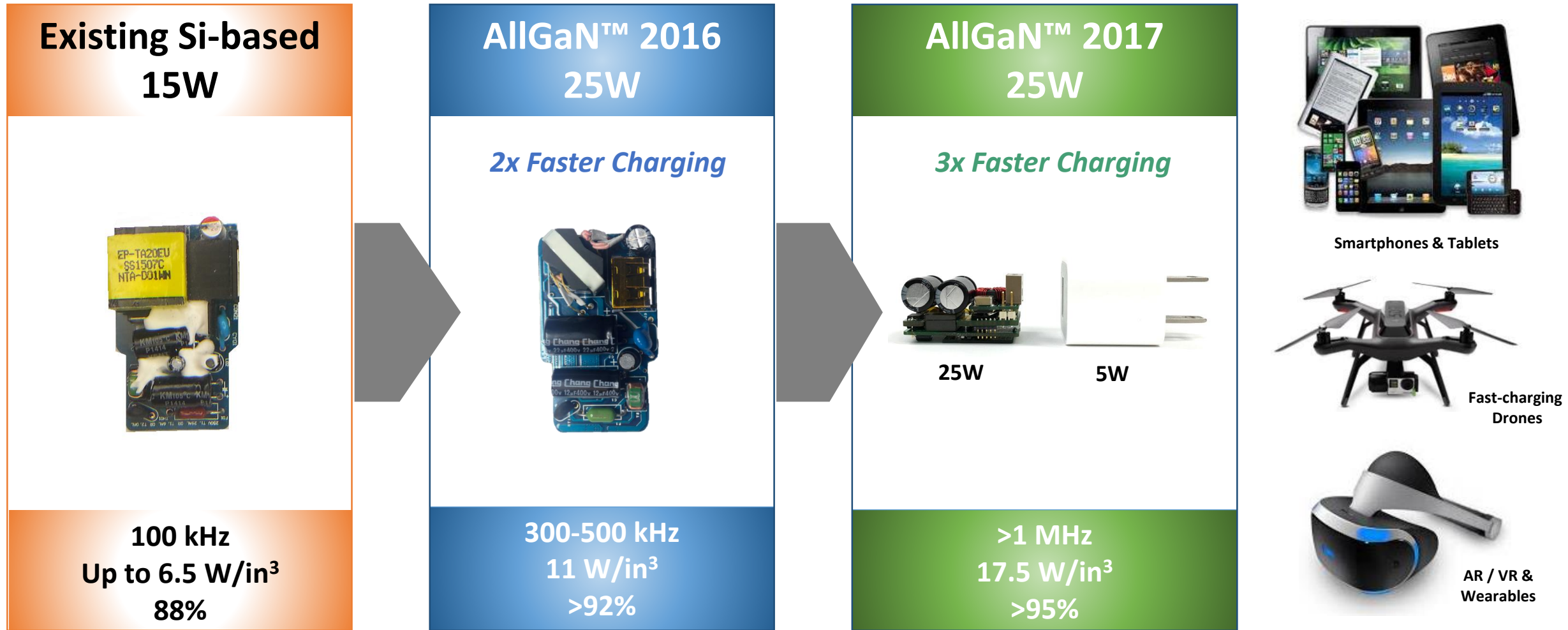

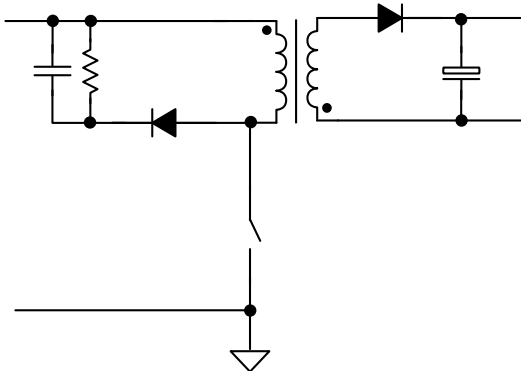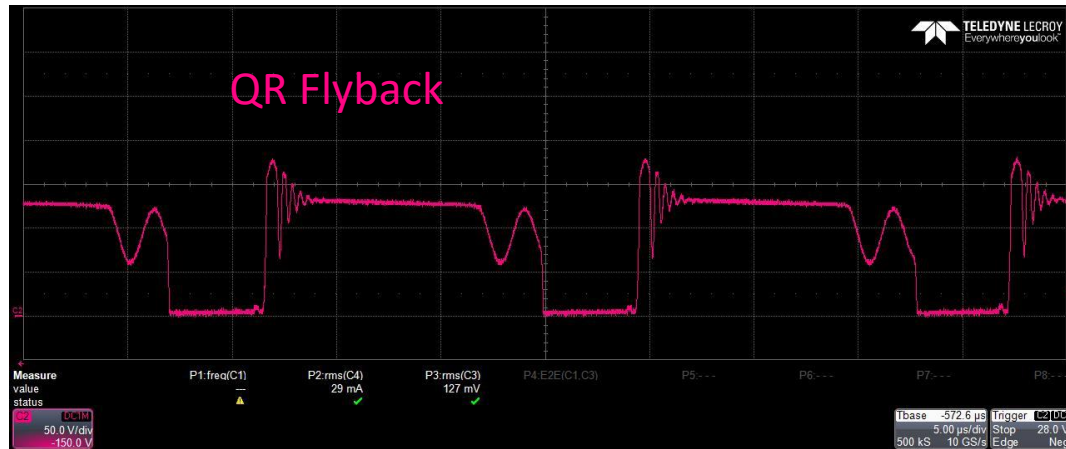Quasi-Resonant (QR) vs. Active Clamp Flyback (ACF)



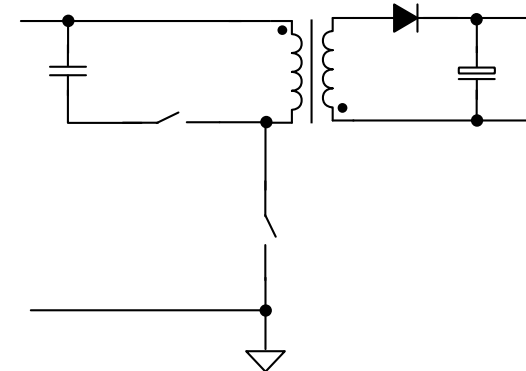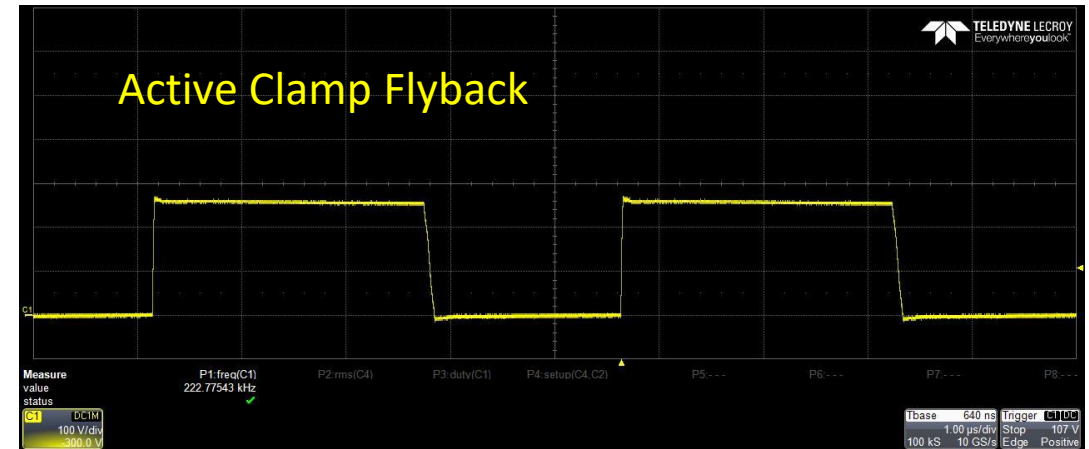- High loss in RCD snubber circuit
- Partial hard switching at high line
- Losses increase with switching frequency




- No resistor needed in the snubber: no snubber loss
- Full range zero-voltage switching (ZVS): no switching loss
- ACF enables high switching frequency


25W ACF: 66% More Power



Original 15 W case


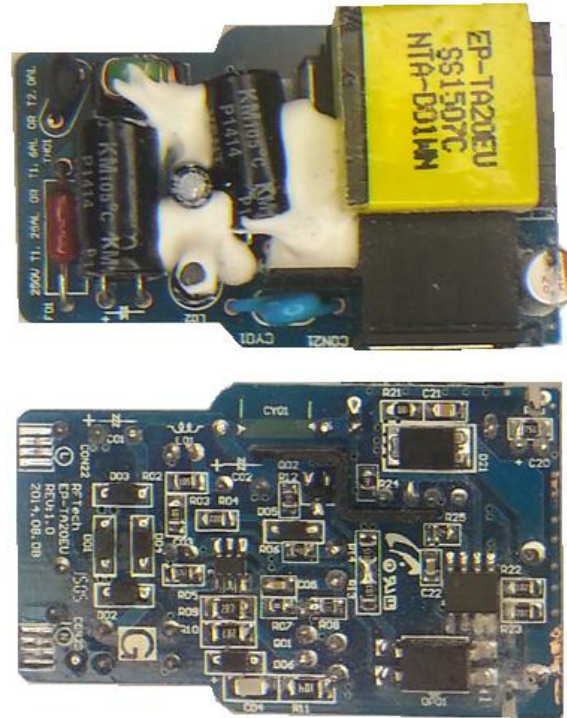


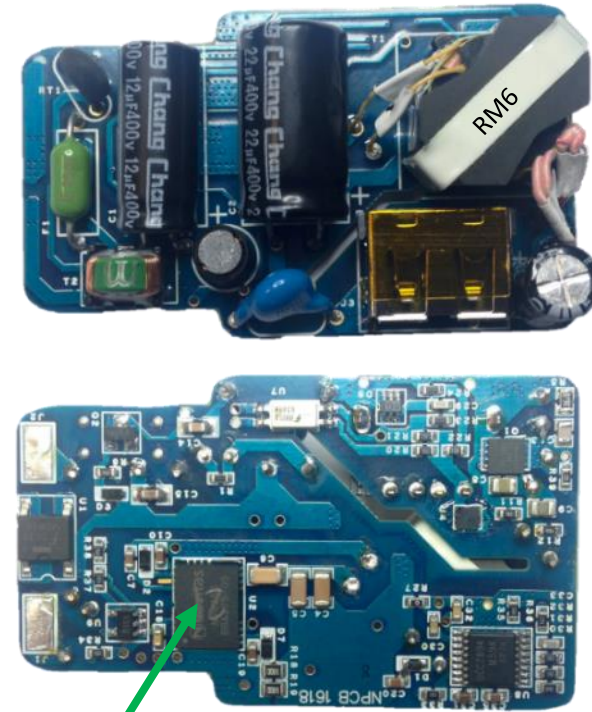Original 15 W
Si-based QR Flyback
~100 kHz




Upgraded 25 W
Half-Bridge GaN Power IC ACF
~400 kHz


45W ACF

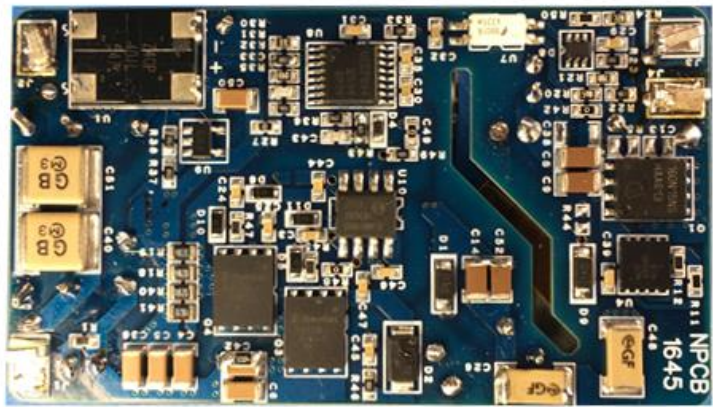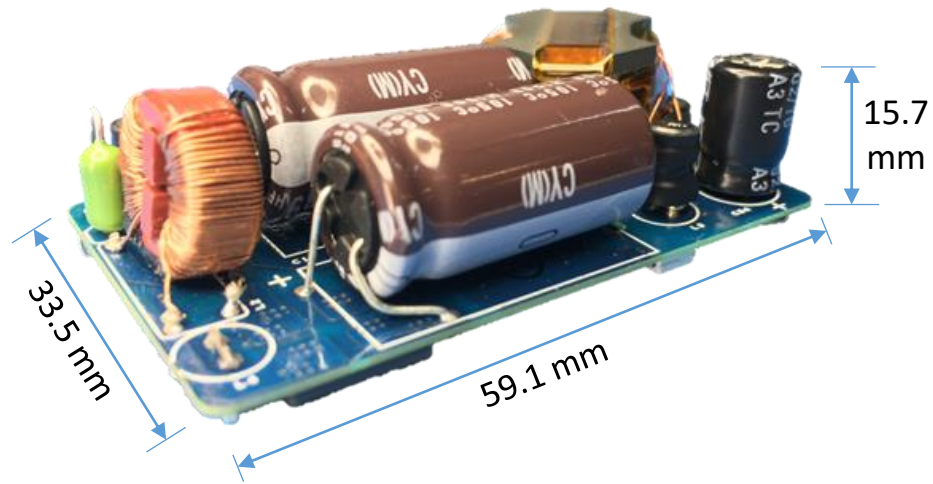

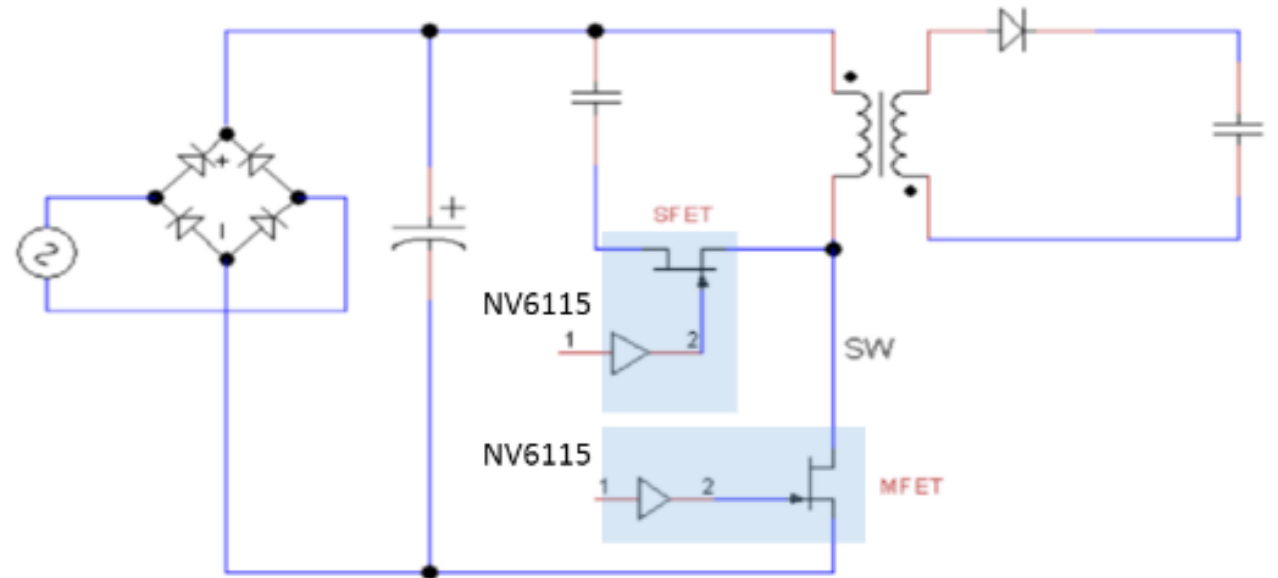- 94.5% efficient at 220V (94.2% at 120V_{AC}, 93.1% at 90V_{AC})
- 23.7 W/in³ density (uncased)
- 15.7mm profile



45W CrCM ACF Operation


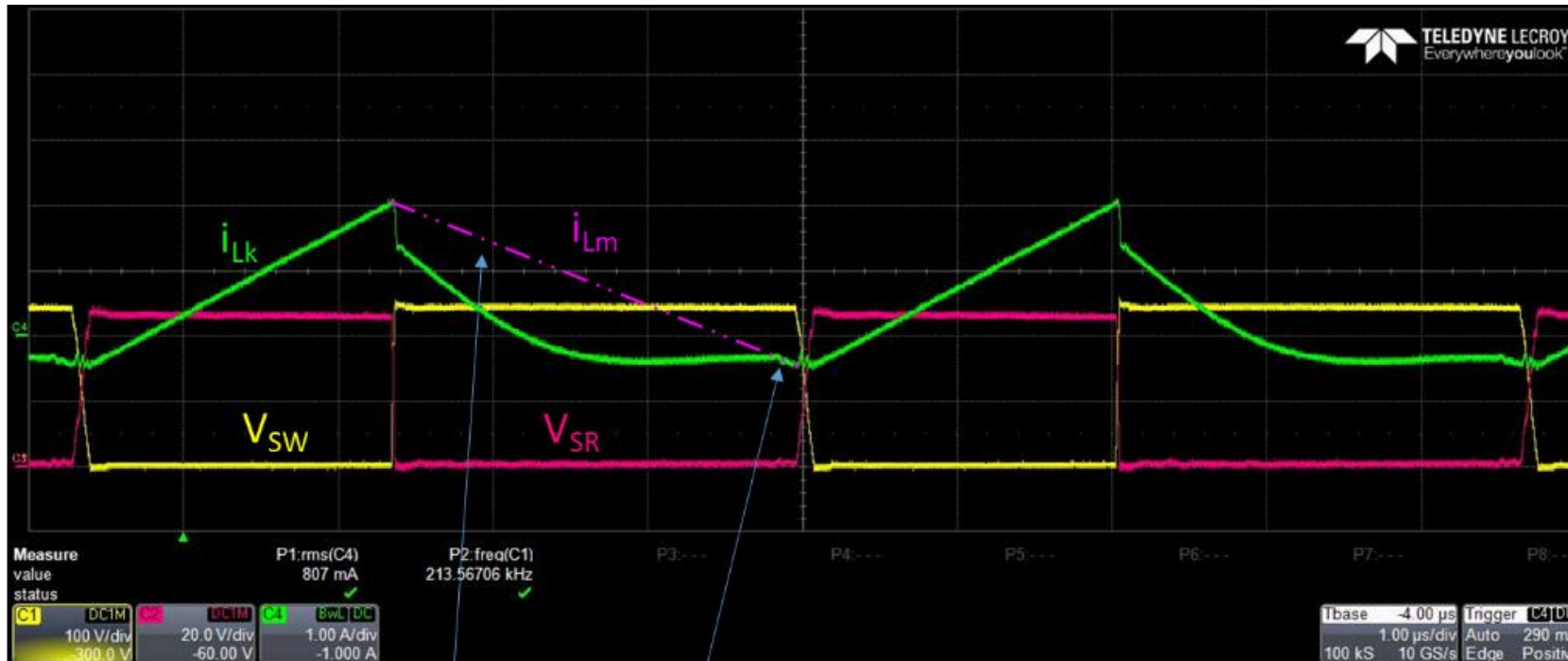


Magnetizing current (drawing)


Inductor current merges with magnetizing current, achieves SR ZCS turn-off

- Switch-node voltage (V_{SW}), SR FET voltage (V_{SR}), leakage current (i_{LK}) and magnetizing current (i_{Lm})
- 120V_{AC}, 0.2A load, $F_{SW} = 210\text{kHz}$

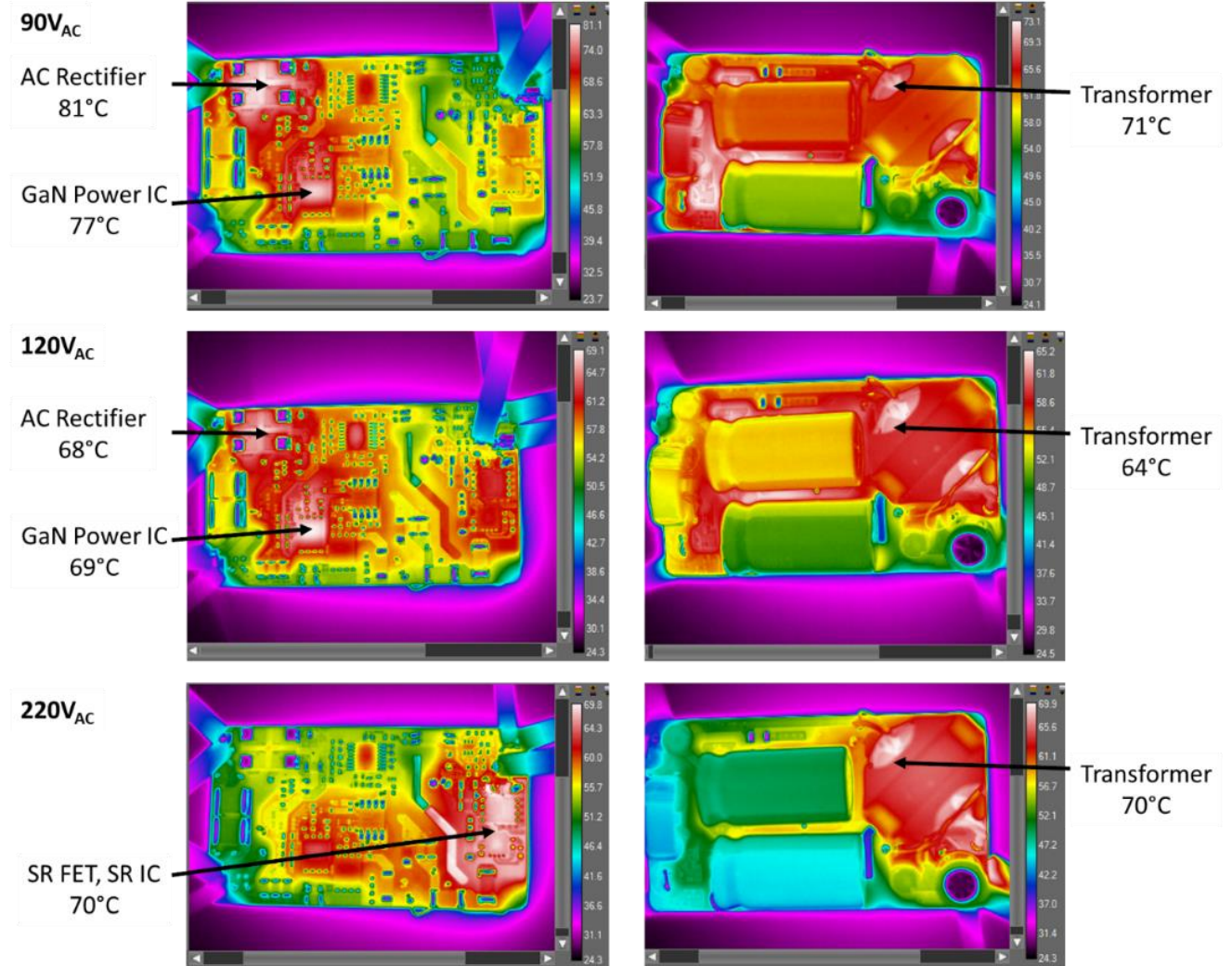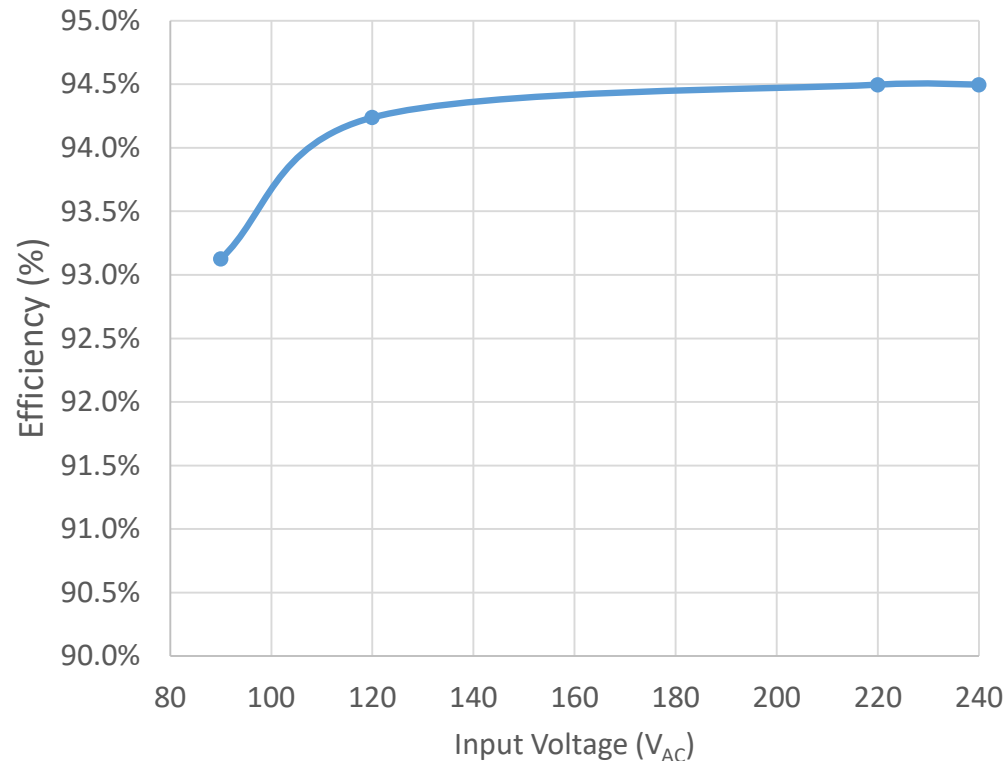45W ACF: High Efficiency, Cool Temperatures



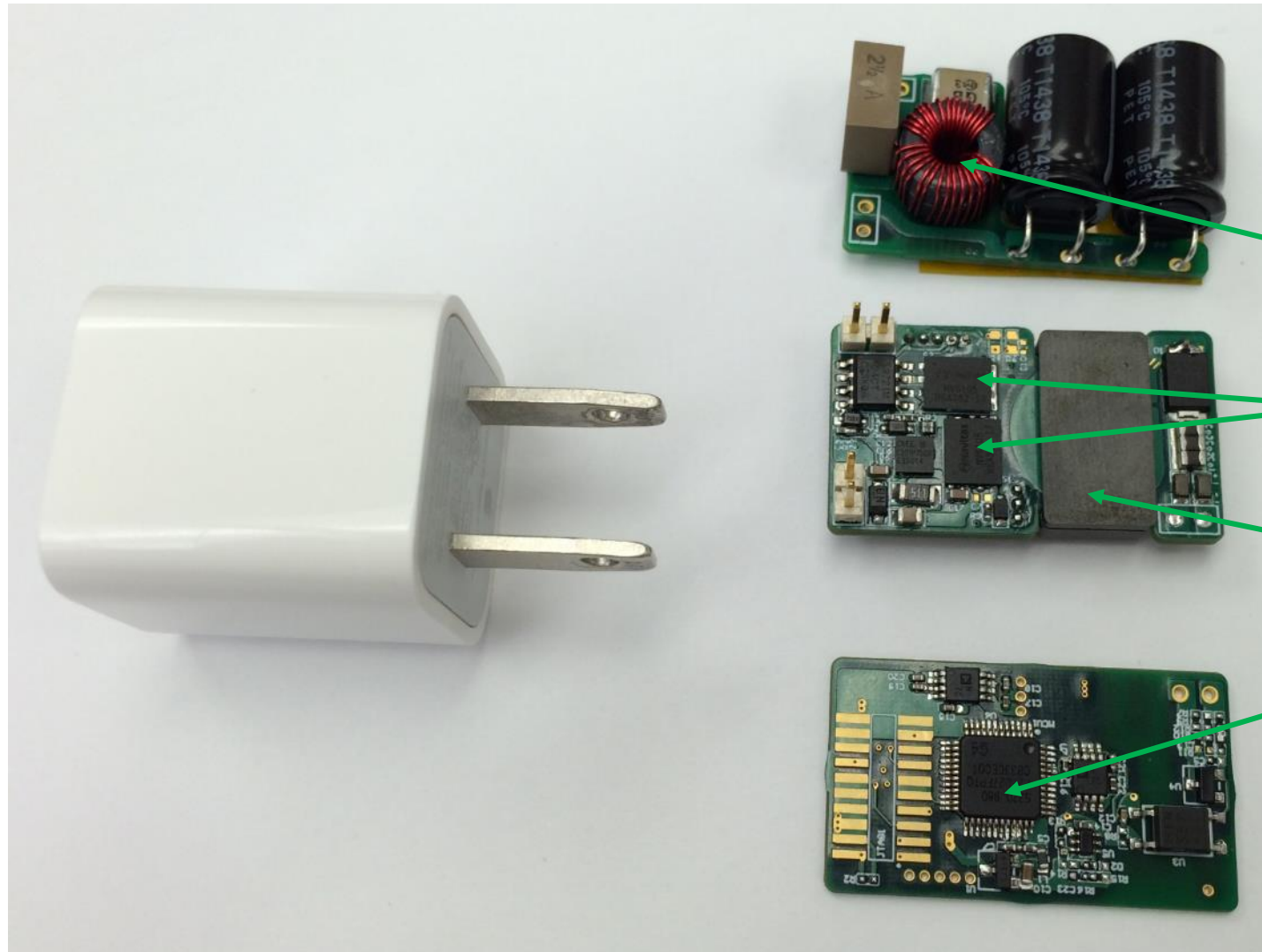
1 MHz, 25 W, 17 W/in³ (cased) ACF (CPES 2016)




- Single-stage EMI
- Navitas GaN Power ICs
- Planar transformer
- DSP (for prototype)

MHz+ 25 W ACF

$F_{SW}=1.5\text{MHz}$

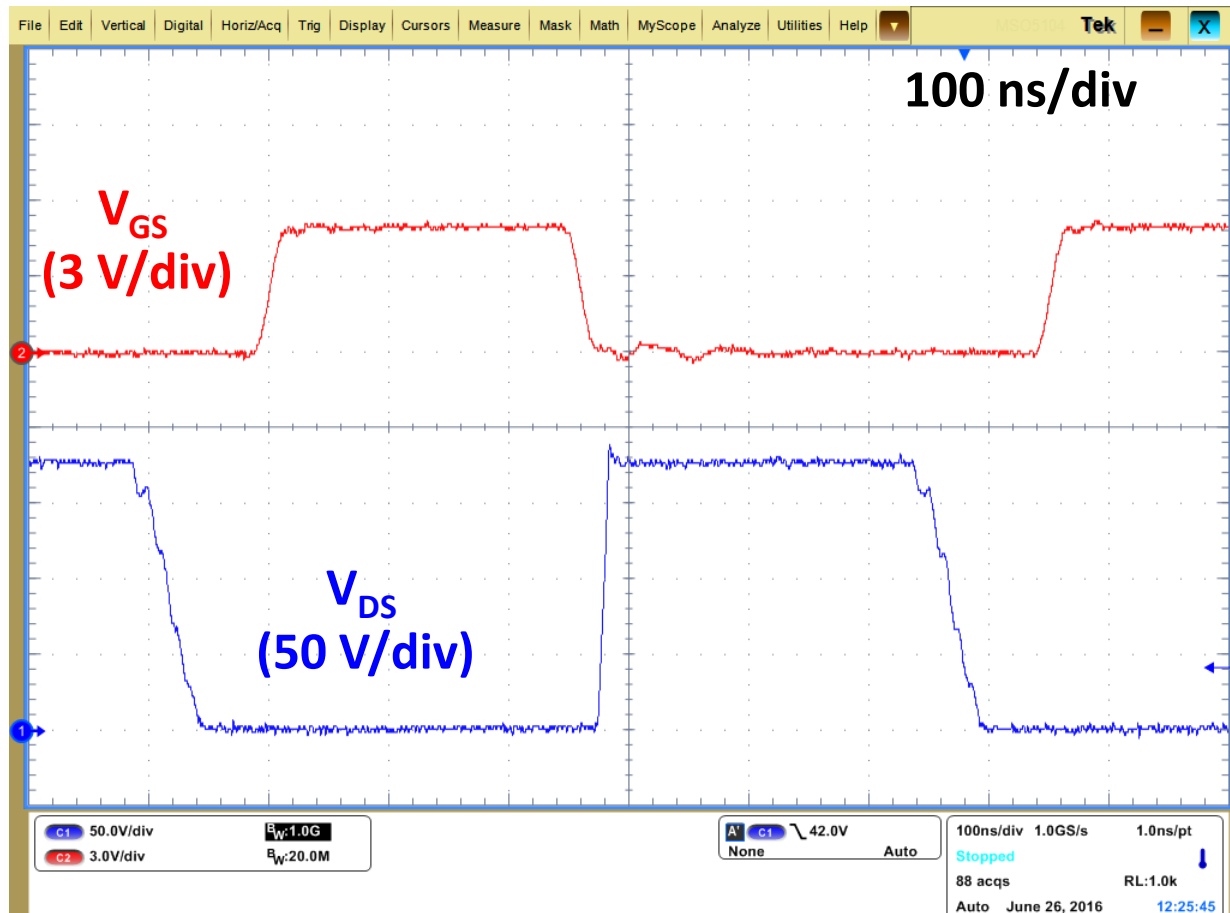

Efficiency vs. Load

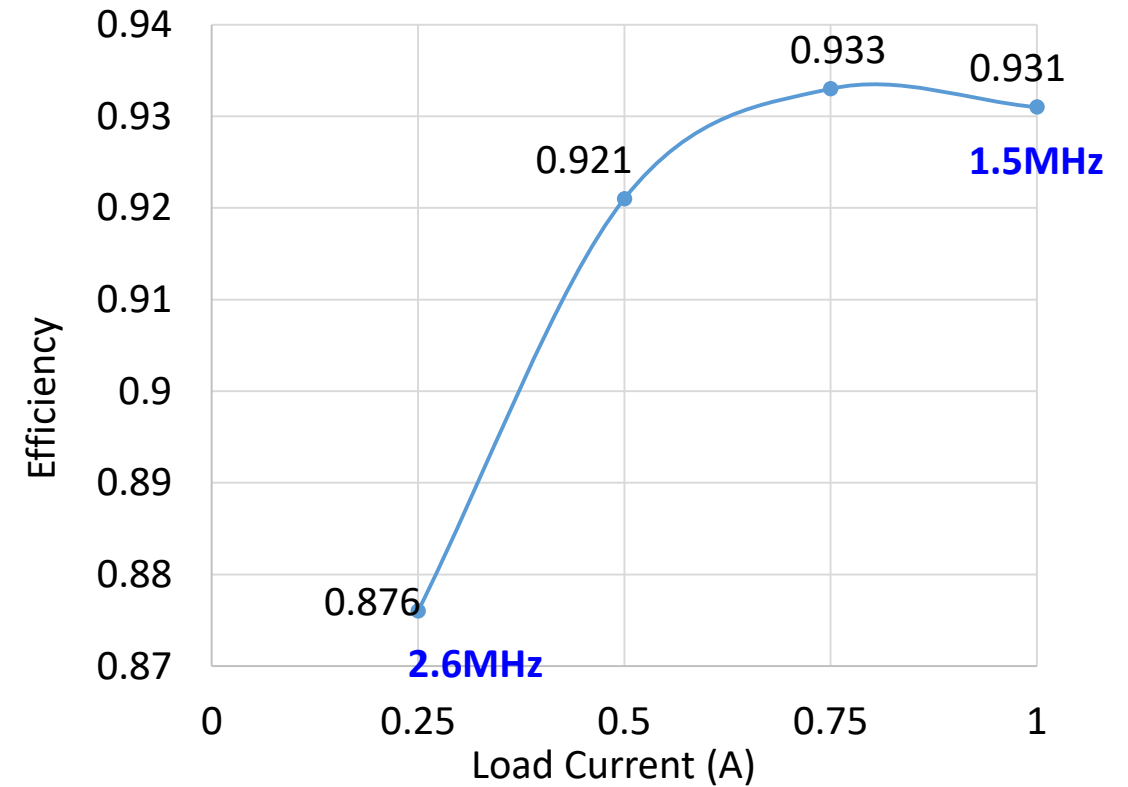

* Exclude bridge and EMI filter loss

GaN Power ICs enable Hi-Density Adapters

3x Higher Density with 50% Energy Savings

**Existing Si-based
150W**



**100 kHz
5-10 W/in³
88%**

**AllGaN™ 2016
150W**

2x Higher Density



**300-500 kHz
17 W/in³
>93%**

**AllGaN™ 2017
150W**

3x Higher Density



**>1 MHz
26.5 W/in³
>95%**




Ultra-thin LED TV

All-in-One
PCs




Next-Gen
Gaming Consoles

150W AC-19V


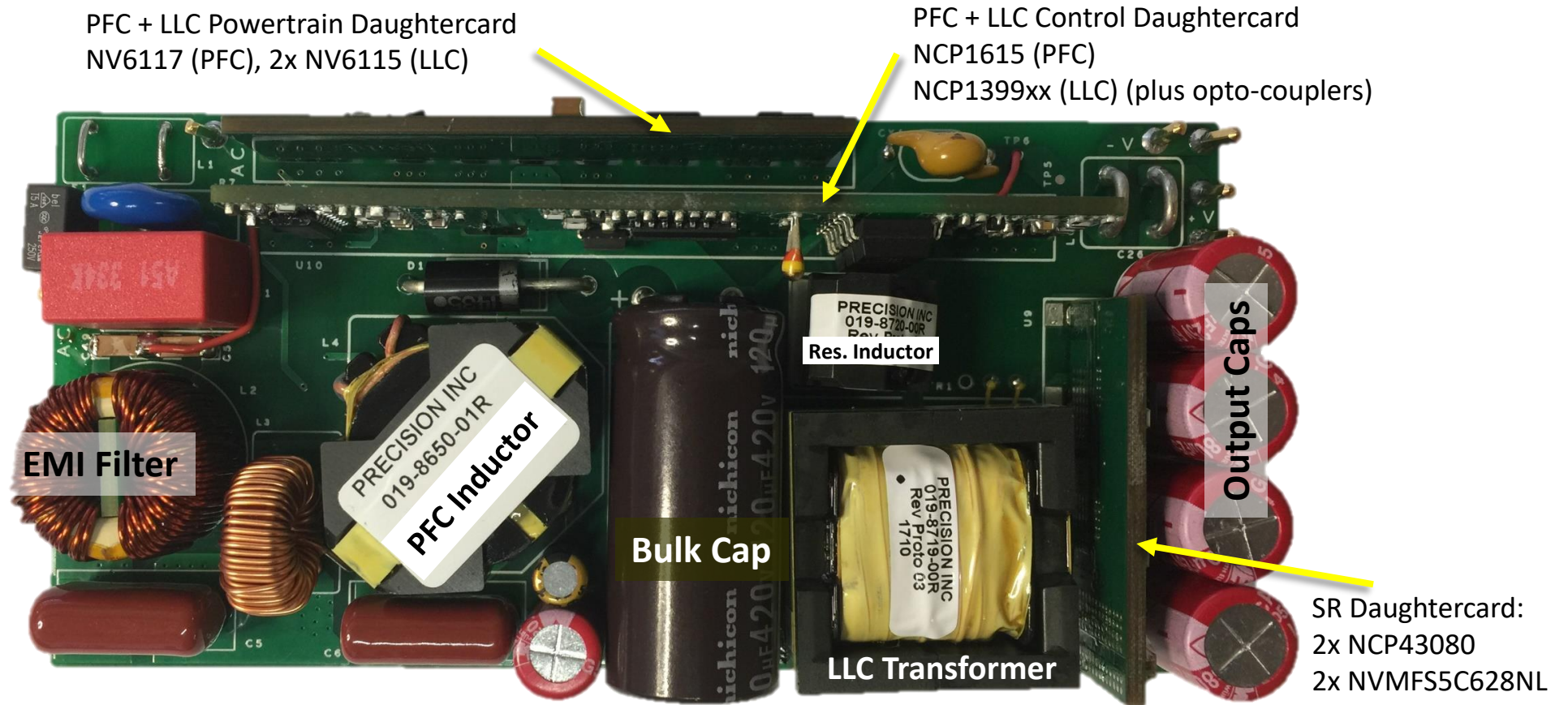


Schematics (Complete Board)

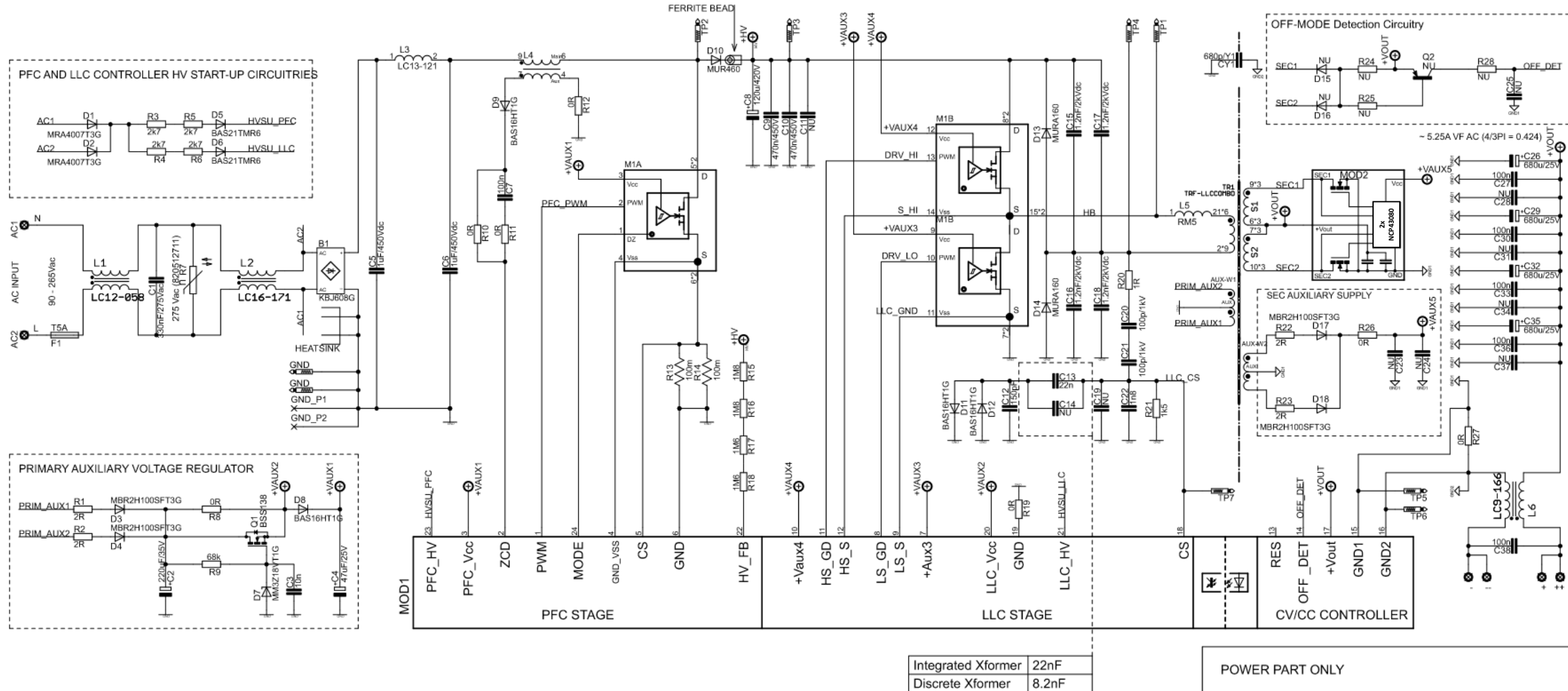


Schematics (Complete Board)

HV Start-Up + X2 Cap Discharge

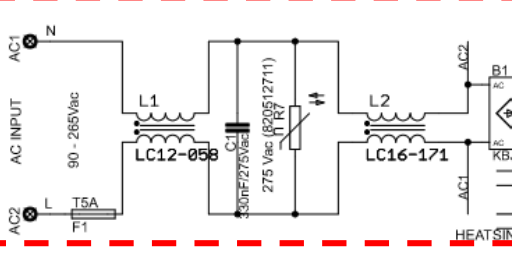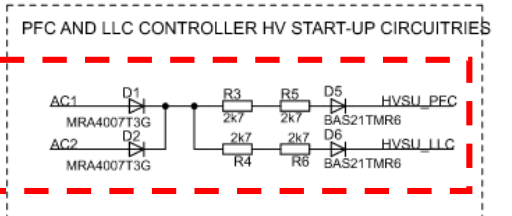

EMI + Rectifier

Aux V_{CC} Supply

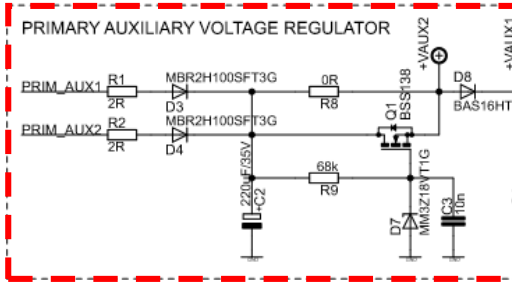


EMI

Boost PFC

LLC

SR + Output Reg

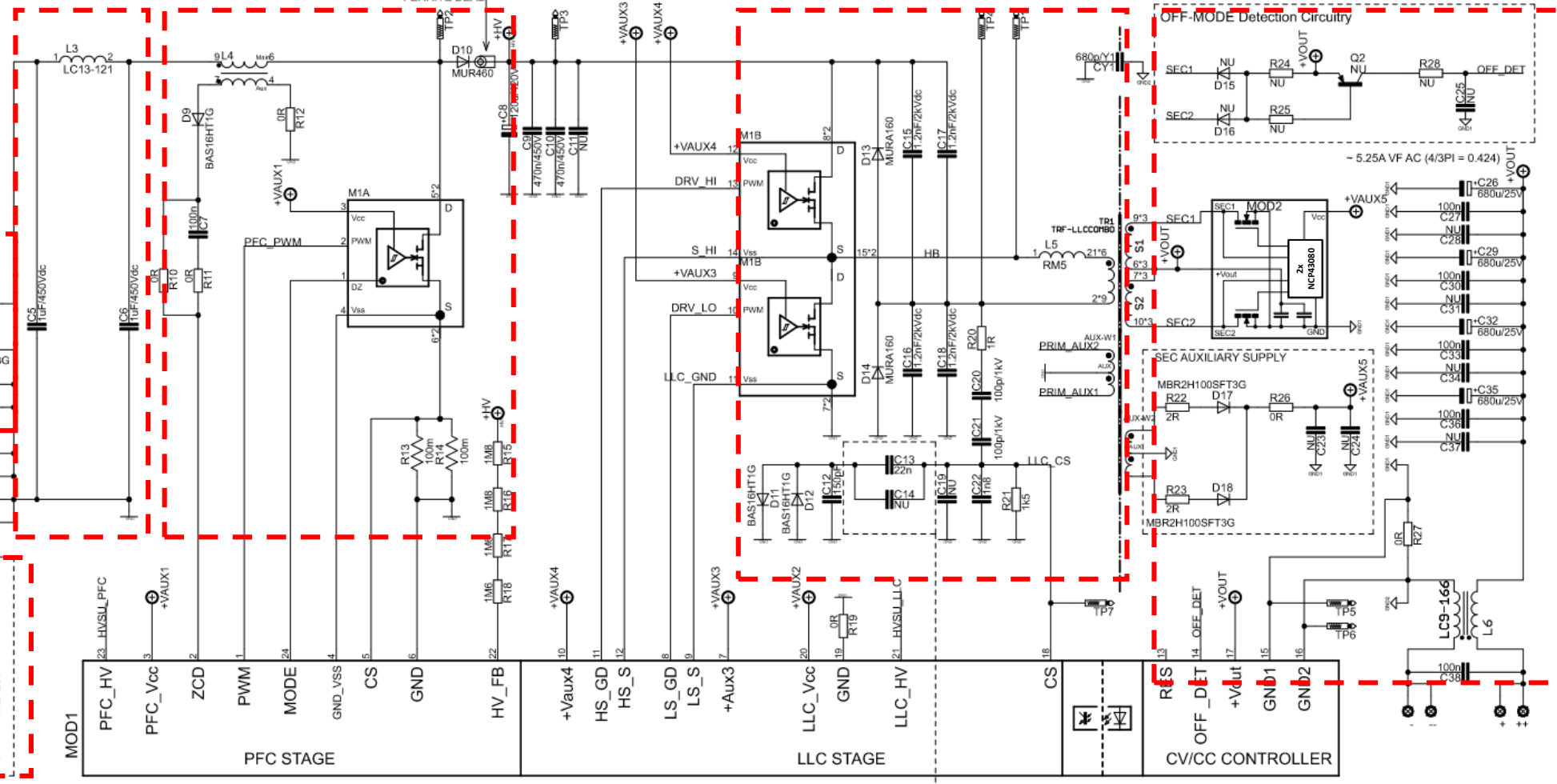


Integrated Xformer	22nF
Discrete Xformer	8.2nF


POWER PART ONLY

PFC Waveforms

PFC FET V_{DS} , LLC V_{SW} at start-up

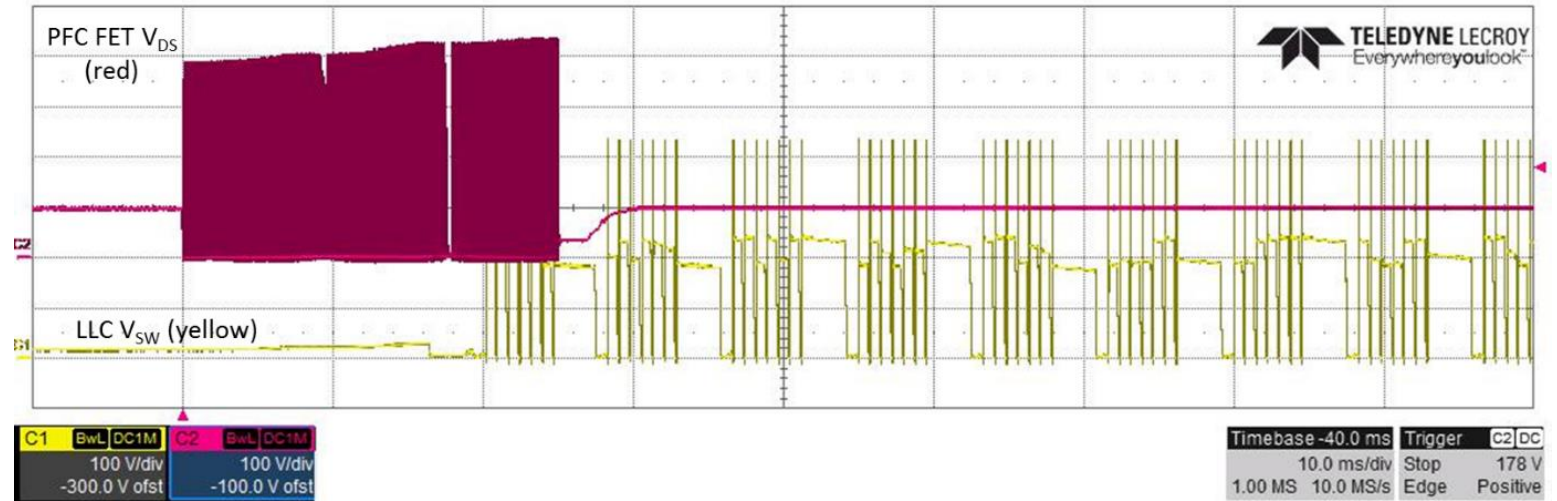




PFC switching (zoom), 220V_{AC}, 150W

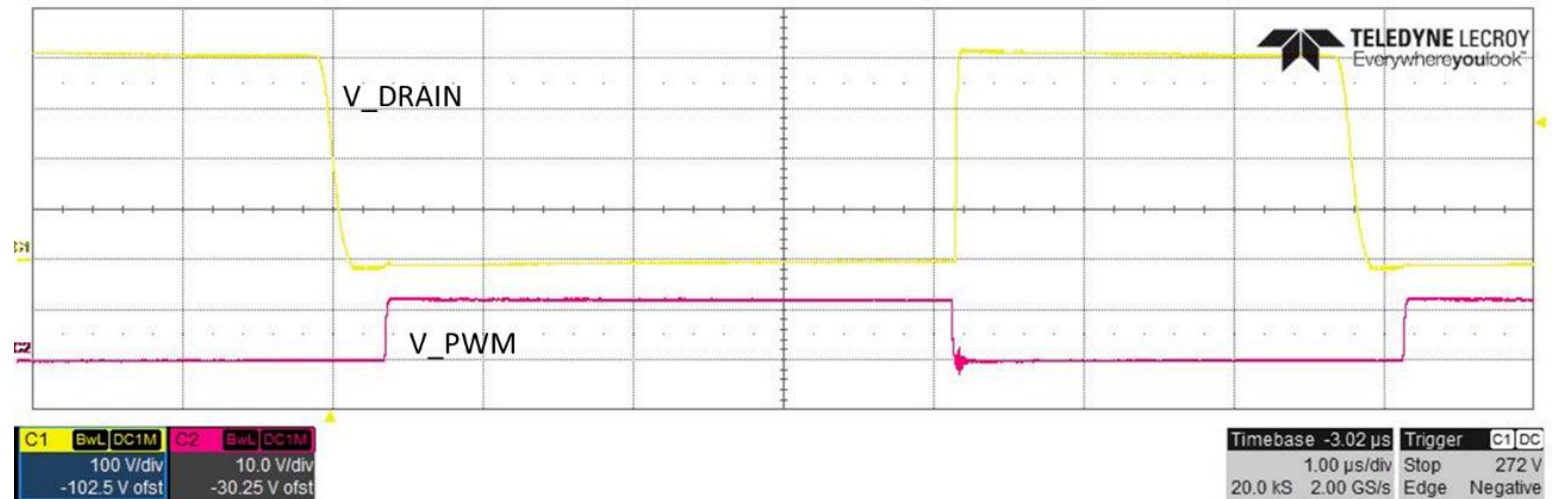



PFC Waveforms

PFC switching (zoom), 220V_{AC}, 150W



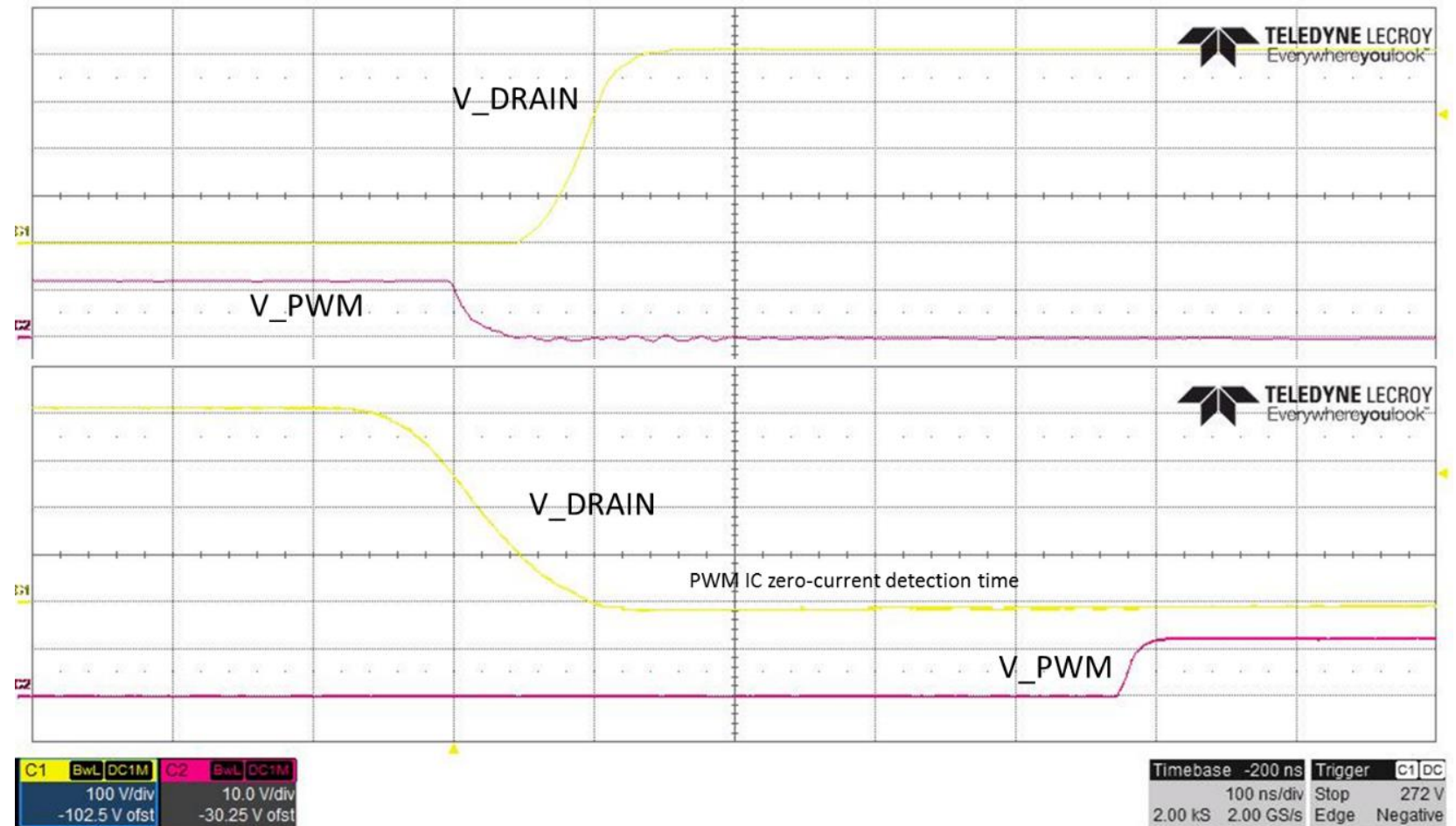


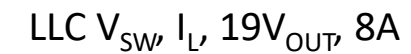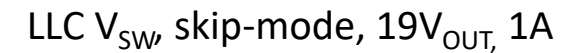

150W: Running Cool

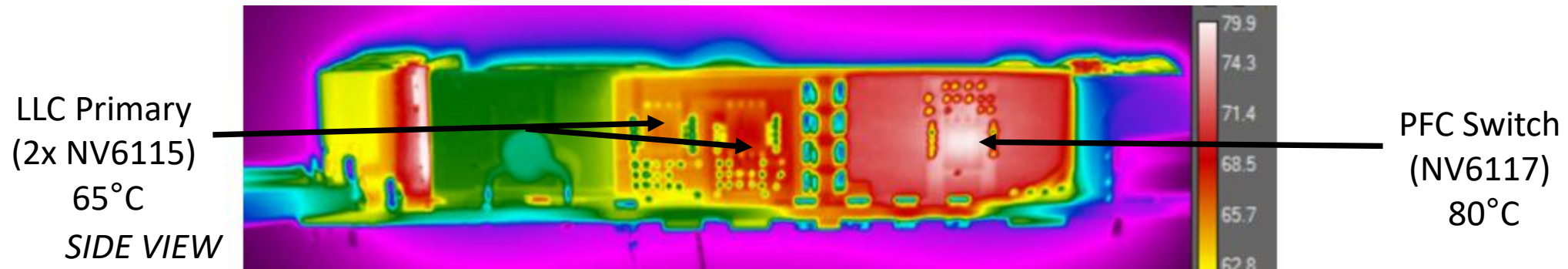
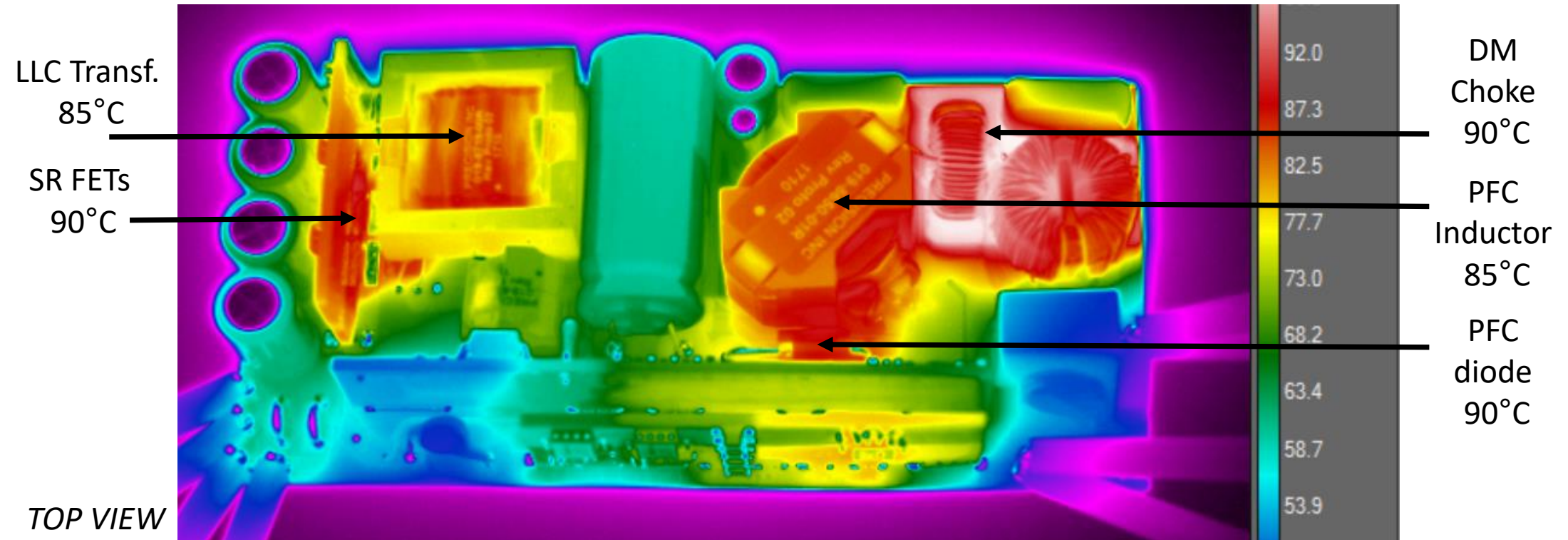


150W AC-19V, ~300 kHz

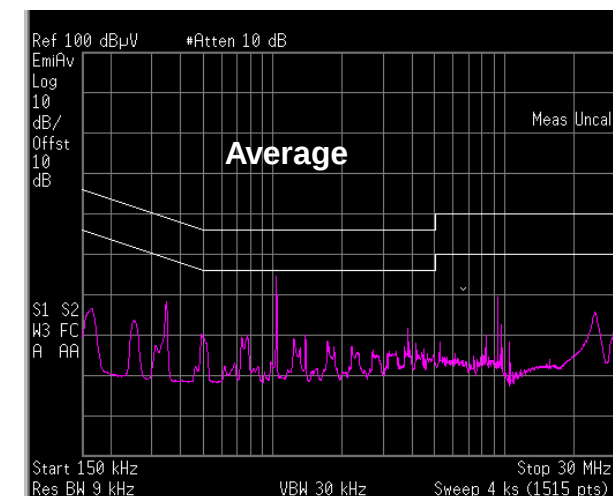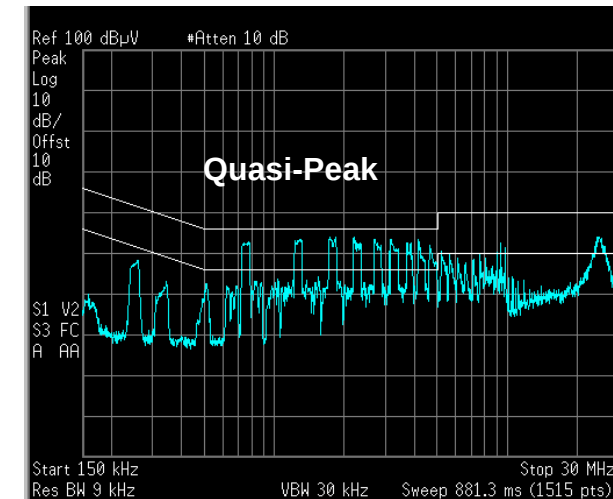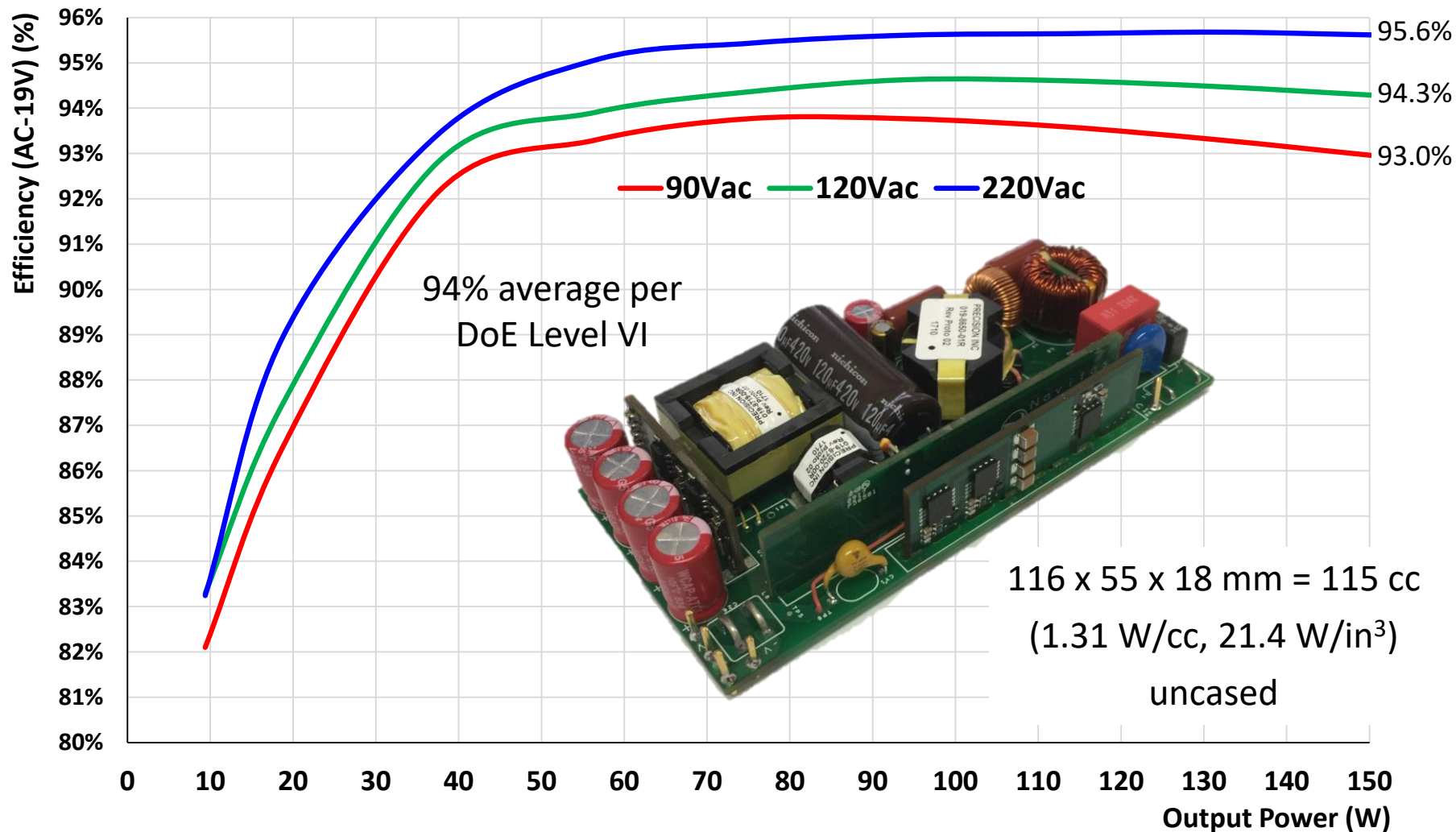


150W, 19V: GaN Power IC vs. Si

Part#	Technology	V	Pack	$R_{DS(ON)}$ (typ. m Ω)	Q_G (typ. nC)	$C_{OSS(er)}$ (typ. pF)	$R \times Q_G$ (m Ω .nC)	$R \times C_{OSS(er)}$ (m Ω .pF)
STL34N65M5	Si FET	650	8x8	99	62.5	63	6,187	6,237
IPL60R199CP	Si FET	600	8x8	180	32	69	5,760	12,420
IPL60R299CP	Si FET	600	8x8	270	22	46	5,940	12,420
NV6115	GaN Power IC	650	5x6	160	2.5	30	400	4,800
NV6117	GaN Power IC	650	5x6	110	4	45	440	4,950
GaN Benefit							14x	1.5-2.5x

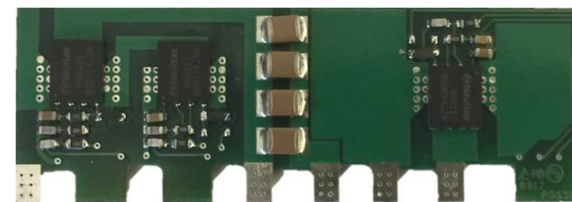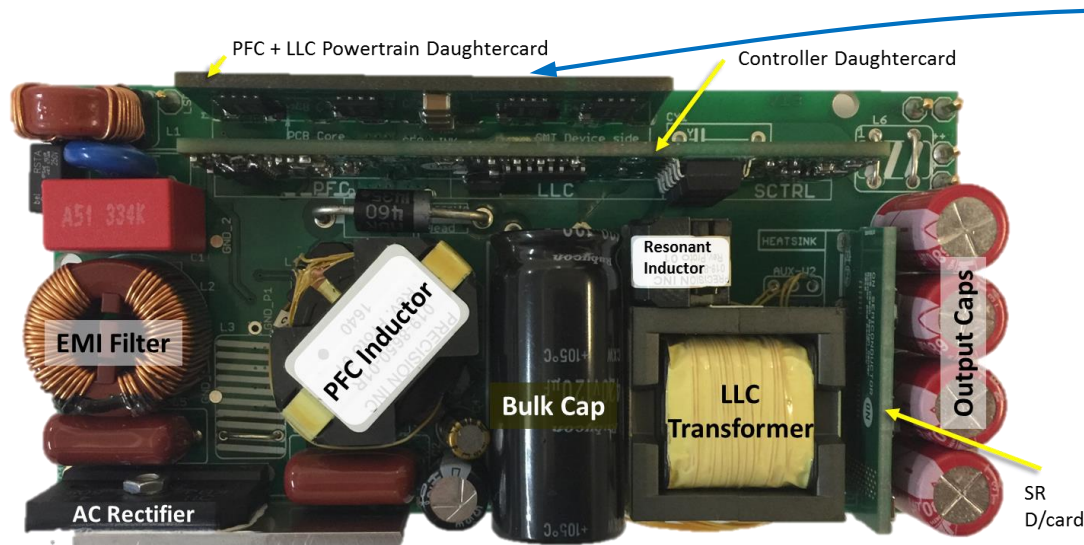

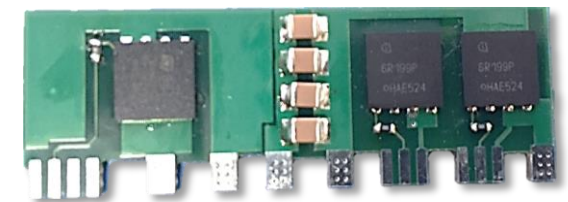Navitas GaN Power ICs (5x6mm QFN)
PFC = 1x NV6117, LLC = 2x NV6115




Si FETs (8x8mm QFN)
a) PFC = 1x IPL60R299CP, LLC = 2x IPL60R299CP
b) PFC = 1x IPL60R199CP, LLC = 2x IPL60R299CP

Si Starts Hard Switching as Frequency Increases



120V_{AC}, Si CP partial hard-switching (~200kHz)

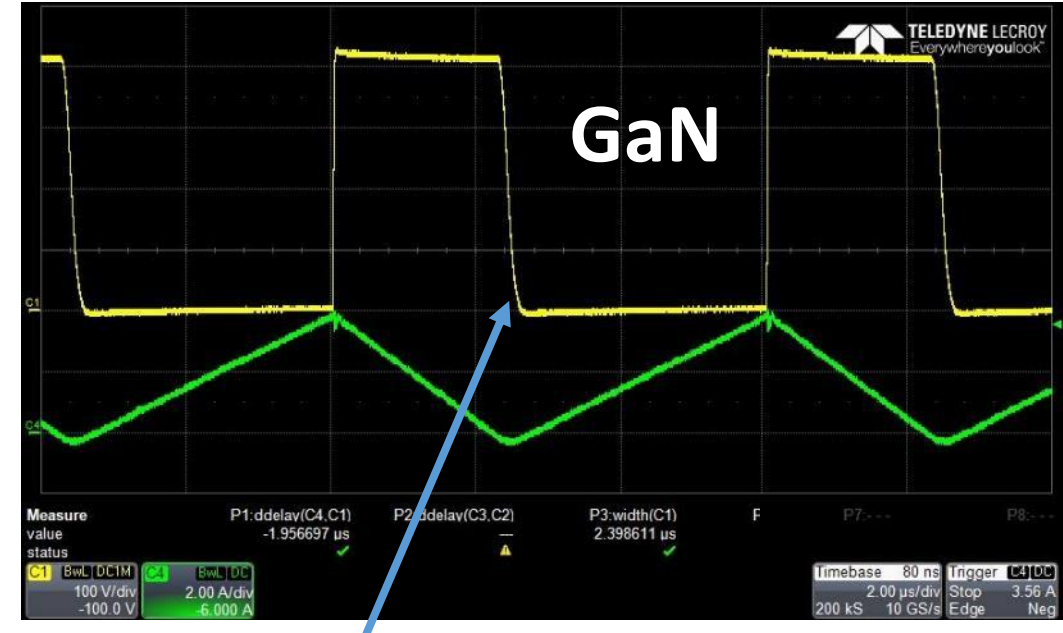- Voltage spikes
- Partial hard-switching (loss)



120V_{AC}, GaN clean ZVS waveforms (~200kHz)

- No voltage spikes / overshoot
- Clean ZVS turn-on transition
- Minimize deadtime for low reverse conduction loss

GaN vs. Si

High Power Density and High Switching Frequency Adapter

ON


- Ultra high-power density up to 22 W/ in³
- Very high Efficiency up to 96 % with GaN Power FETs
- The smallest dimensions 4.6 x 1.96 x 0.78 in
- Performance ensured by NCP1399, NCP1615, NCP43080
- Up to 94 % Efficiency with Silicon Super-Junction MOSFETs

Typical applications

- High Power Laptop Adaptors, Power supplies, Power chargers
- 150 W Output Power @ 19 V with ~8.5 A current limit



Efficiency = 94%, 13W/in³

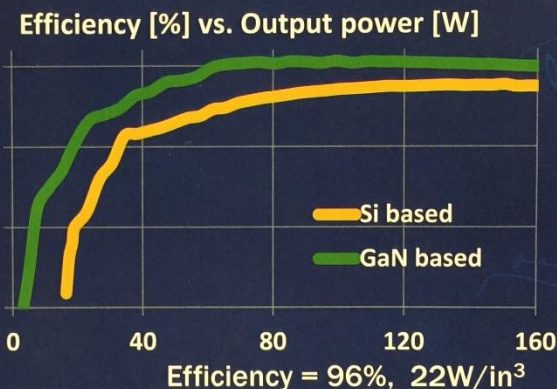


Higher switching frequency enables:


- Up to 40% volume reduction, Power Density almost doubled
- Compact design / balanced price
- Keep high efficiency

MHz 150W Totem-pole + LLC (CPES 2016)



PFC

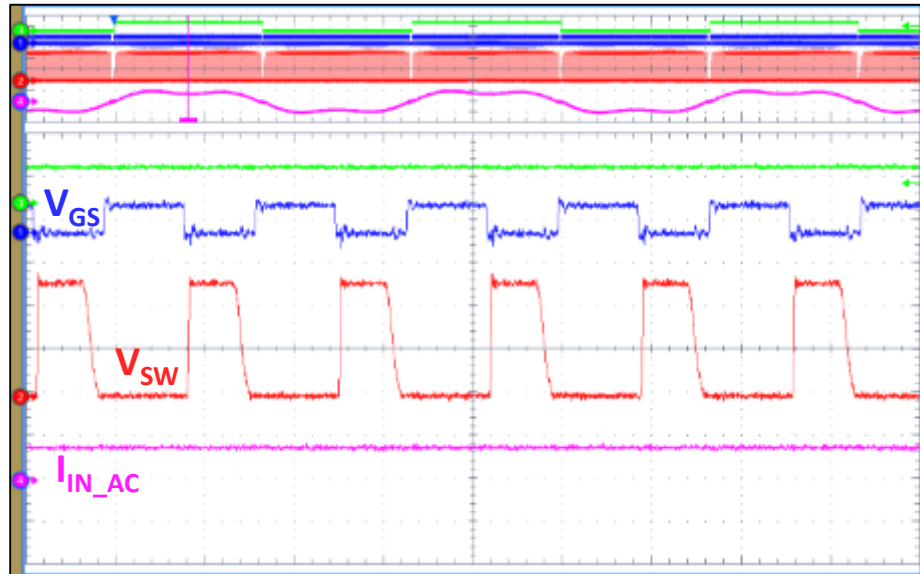

LLC

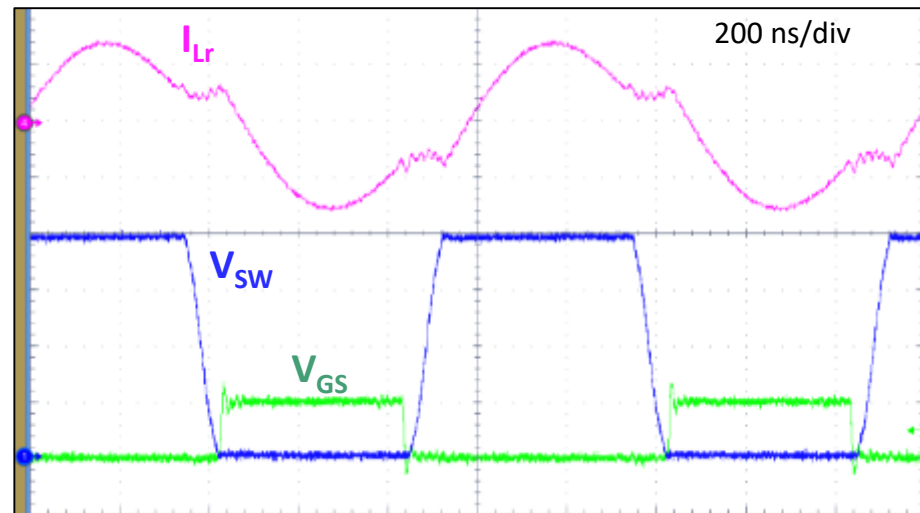

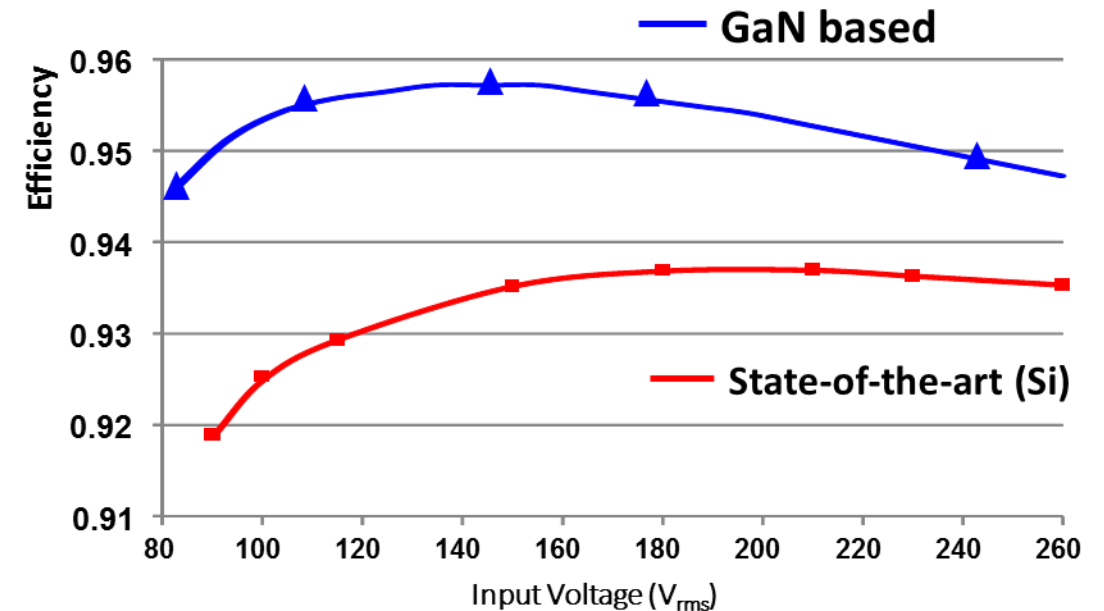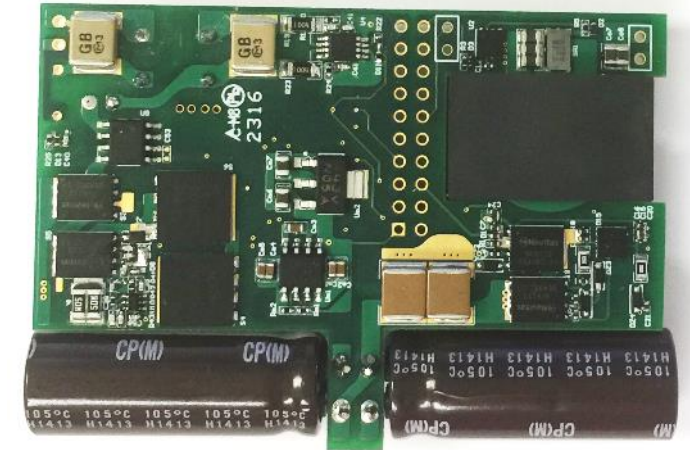GaN-based
Power Density
= 35 W/in^3
(uncased)



Pop Quiz! How do we shrink our power supplies?

- A. Select the right ZVS topology
- B. Increase switching frequency
- C. Select the right magnetic material
- D. Select the right GaN Power IC
- E. Increase efficiency
- F. **All of the above**
- G. None of the above...
...use hard-switching topologies and Silicon switching < 100kHz.